

Cobra Uniden Antenna Amplifiers Microphones Cb radio reviews modifications



Cobra Uniden Antenna Amplifiers Microphones Cb radio reviews modifications

Resurrecting a Dead D-104

Article written and submitted by Hambone



I got a good deal on a nice-looking D-104 T-UG8 but could NOT get rid of the RF feedback, no matter what I did. I put a FET in front of the existing preamp, replaced the preamp with an entirely different circuit, and hung bypass caps on everything-- nothing helped.

I finally decided the crystal element was the culprit - if for no other reason than it was the only thing left besides the switch!


So I replaced it with one of the small, cheap, easy-to-find electret condenser elements. I've used similar mic elements for years in contact mics for musical instruments in performance settings, and knew that they're capable of excellent sound and high output. Here's how it went:

Don't be afraid to take a D-104 apart, the mic element is just a round disk held in place on the round frame by two rubber pieces that wedge in between the element and the frame. It's about 3/8" thick, so a piece of 3/8" plywood does the trick:

The D-104 switching takes a little head-scratching with its break-before-make contacts, but in the TUG-8 at least it's just a DPDT.

The way to wire the switch depends on your radio-- it was more of a pain in the butt for me because my radio required that the mic ground and the PTT ground be kept separate.


One side of the wood was spray-painted flat black (you won't be able to see the back side), and I used the paint-drying time to figure out the switching. Then I hunted up a scrap piece of circuit board and soldered a \$2.99 Radio Shack condenser mic element to the board and soldered the wires that had been attached to the crystal D-104 element to the condenser element. I probably should have drilled a hole all the way through the plywood and brought the wires in from the back, but I didn't think about that until I'd already done it this way:

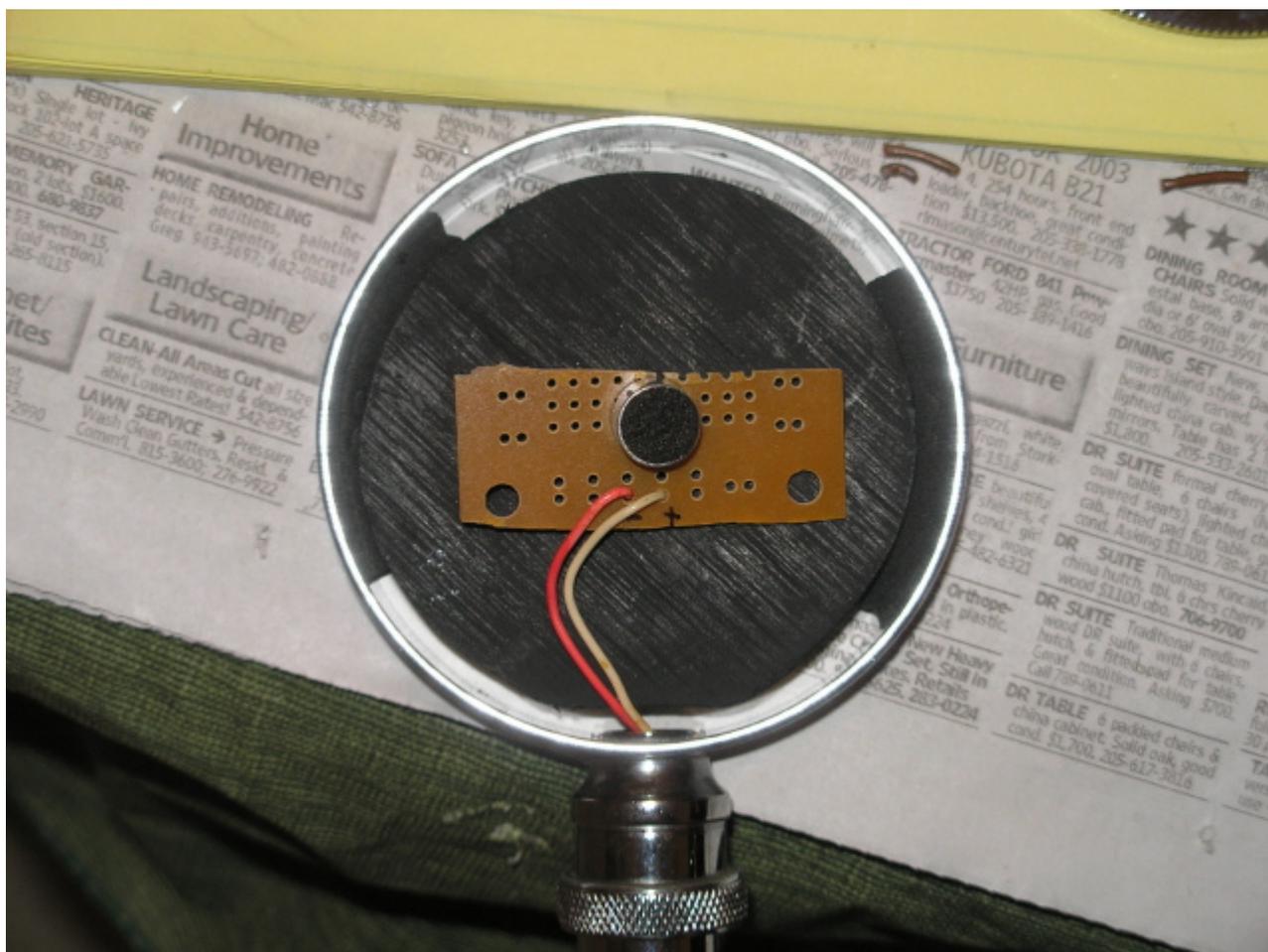

I scooped out a little of the wood behind the circuit board with my Dremel so the board would lay flat against the wood, and then hot-glued the circuit board to the wood-- and then took a foam earpiece off an earbud and hot-glued it around the element to act as a pop filter. The final step was to color the circuit board black with one of those big Sharpies so it wouldn't show through the D-104 screen. These small electret condenser elements are very susceptible to breath pops, and depending on how close you prefer to have the mic to your mouth, a thin earbud foam may not provide enough of a windscreen. If that's the case, find a windscreen for a normal PA mic and cut off the front end to fit within the grille of the D-104. That's what I eventually did to mine.


So- how does this work? Very well! My radio (an Icom-- no, it's not on 27 MHz) needs a fairly hot mic level so I ended up building a simple preamp for it, but most radios probably will not need it. The preamp was built on a small piece of circuit board, and mounted on top of the terminal strip in the mic's base, using the two screws already there. Try it without the preamp first. The electret elements have a built-in preamp, and are capable of surprisingly hot output levels. The back of the

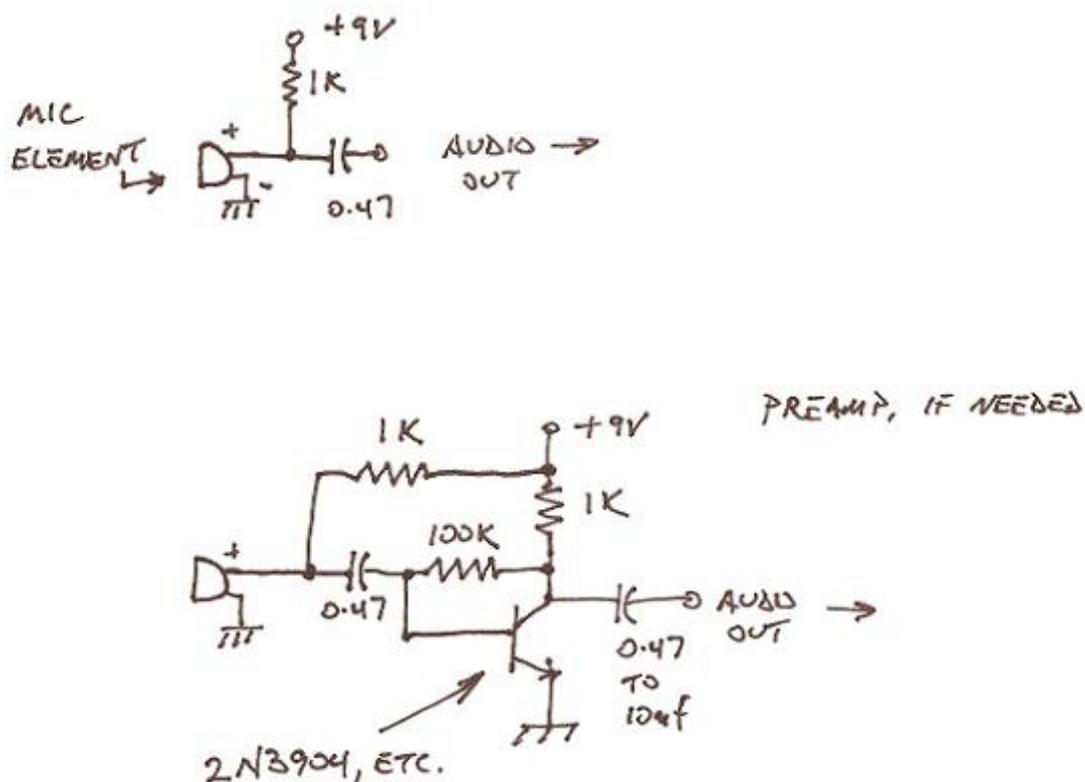bubble pack card shows the resistor and capacitor you'll need to make it work. In case you need a preamp, here's what I used:



The low impedance element matches up great, and would to any low impedance radio. It doesn't -sound- exactly like a D-104, but you can change the high/low freq response by changing the value of the capacitor to a lower value-- it will work with just about anything up to 20 uf, but that sounded bassy and mushy on my radio. I settled on a 0.47 uf, which gave it a lot more "cut" without being too tinny. You can use that value or experiment with several to get the tone that suits your voice best.

If you want to get fancy you may be able to power it directly from your radio, but I used the 9V battery it had been using anyway-- that allowed me to still use the 4 conductor cable. I'm going to look around for a non-working D-104 I can get cheap and do the same for my Galaxy. The existing volume control was also used since it's already there and can be accessed through the bottom cover. If the output of the mic is too hot, wire the mic's output to the top terminal, ground to the bottom terminal, and the audio lead of the mic cable to the middle terminal. You'll definitely want to use the pot if you use a preamp circuit:

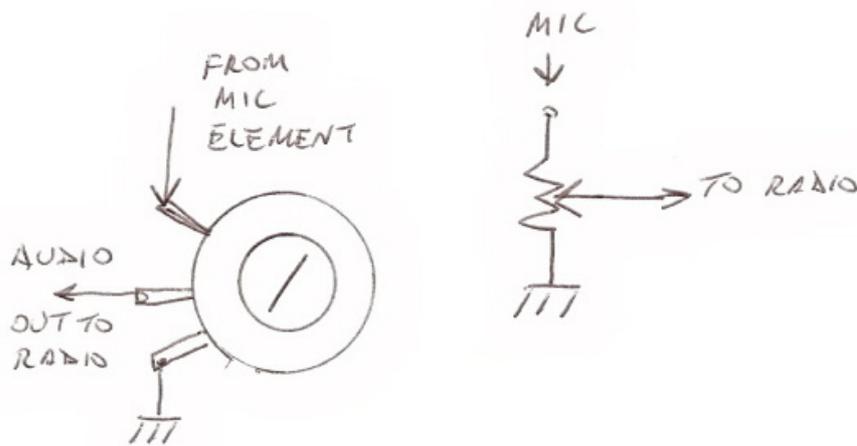

The same thing can be done for just about any mic, such as the Turner +2, Shure 444, and most hand mics. For these mics a piece of circuit board cut to fit inside the chassis may do the trick without having to use a piece of wood, but it's not critical-- whatever works, just make sure it doesn't rattle around the contacts aren't able to touch the chassis of the mic. Switching the battery to the element and the PTT will be slightly different for each mic, but should not be too hard to figure out.

So if you have a vintage mic you'd like to put back into service, or if that Ebay Special doesn't *quite* work, give this approach a try. It's not expensive, and it's fun to use a microphone that you rebuilt yourself- and they sound great!

Good luck and 73's,

Hambone

Cobra Uniden Antenna Amplifiers Microphones Cb radio reviews modifications

Cobra Uniden Antenna Amplifiers Microphones Cb radio reviews modifications

This website is purely for entertainment purposes. Any and all articles, reviews, products, pictures, writings or any other material published on this website are written and are to be used for entertainment purposes only. All materials on this website are written and posted purely to entertain the reader/website visitor. All opinions, articles and written statements on this website are opinion. Anyone visiting and viewing the material on this website agrees that the content on this website is to be used for entertainment purposes only. This website does not condone or take part in illegal activities and can not be held responsible for any illegal acts committed by anyone including visitors or any other persons who may read or see or hear about any content from this website. Since this website's content is purely for entertainment and is purely for entertainment purposes we refer anyone seeking information regarding any electronic devices governed by the FCC including CB radios to visit the website of the Federal Communications Commission. For factual information regarding Citizens Band radio rules and operation please visit the FCC website at http://wireless.fcc.gov/services/index.htm?job=service_home&id=cb. The FCC is a government factual source for legal rules and information on how to buy, use, and operate a CB radio.