

Assembly Manual

Mini 1.5V to 9V DC Converter

(PCB and components only)

PLEASE READ DISCLAIMER CAREFULLY AS WE
CAN ONLY GUARANTEE PARTS AND NOT THE
LABOUR CONTENT YOU PROVIDE

Reproduced in part by arrangement
with Silicon Chip, from their August
1992 edition.

K-3231

DICK SMITH
ELECTRONICS

ACN 000 445 956

K I T

This tiny project allows you to replace those expensive 9V batteries with more cost-efficient 1.5V cells. It uses only three components and is smaller than the 9V battery it replaces.

Back in the November 1990 issue of Silicon chip, we published our smallest project ever (DSE Cat.No.K-3230). It used just three electronic components and allowed a 1.5V cell to replace a more expensive 9V battery. You could use any type of 1.5V cell as well - either AA, C, D, N or AAA.


Of course, the bigger the cell, the longer it lasted.

There was just one drawback - the unit was larger than a 9V battery which meant that it could not be fitted inside the device to be powered. This revised unit overcomes that problem by using a much smaller toroid core and a revised PC board. It now measures just 17 x 43 x 16mm which means that it will fit comfortably inside a 9V battery compartment.

The new toroid core is cheaper than the original unit too, which means that the new unit costs a few dollars less than the previous version.

Circuit diagram

Fig.1 shows what's inside the TL-

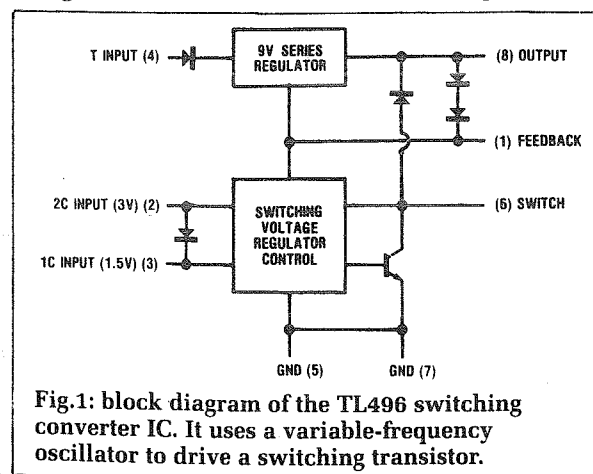

496, while Fig.2 shows the circuit details.

At the heart of the circuit is IC1 which is a TL496CP switching inverter. We gave a detailed explanation of how this IC works in the November 1990 issue, so we'll just briefly cover the circuit operation here.

Inside IC1 is an oscillator that drives a switching transistor at a rate that depends on the load current. The higher the load current, the higher the switching frequency, which can be anywhere from a few Hertz up to 2kHz.

This internal transistor alternately switches the current through inductor L1 on and off. When the transistor is on, current flows and energy is stored in the inductor. When the transistor turns off, the voltage across L1 rises and the inductor dumps its stored energy into the 220µF capacitor.

An internal feedback and voltage regulator circuit ensure that the output is maintained at 9V. The maximum output current which can be

drawn from the circuit is about 40mA. At this current, a typical 9V battery would not last long at all.

By contrast, a 1.5V alkaline D-cell will last for about 20 hours, despite the considerably higher input current required.


Note that because the circuit steps the voltage up six times (from 1.5V to 9V) and because the circuit is not 100% efficient, the current consumed goes up by a factor of twelve (eg, if the load current is 2mA, the input current is 25mA).

Putting it another way, the circuit is about 50% efficient, since the input current goes up by a factor of twelve, not six. Even so, it is still cheaper to use the converter than a 9V battery.

Construction

The PC board for this project is coded SC11111921 and measures 3 x 17mm. Fig.3 shows the assembly details.

The inductor consists of two layers

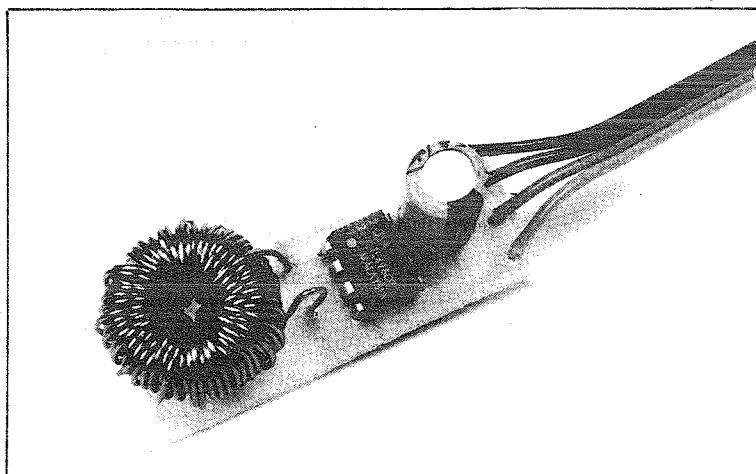

Parts List


- 1 PC board, code SC11111921, 43 x 17mm
- 1 Neosid 17-732-22 toroid core, 14.8 (OD) x 8 (ID) x 6.35mm (H)
- 1 Hookup wire
- 2 metres of 0.63MM enamelled copper wire

Semiconductors

- 1 TL496 DC converter (IC1)

Capacitors

- 1 220uF 16/25 PC electrolytic

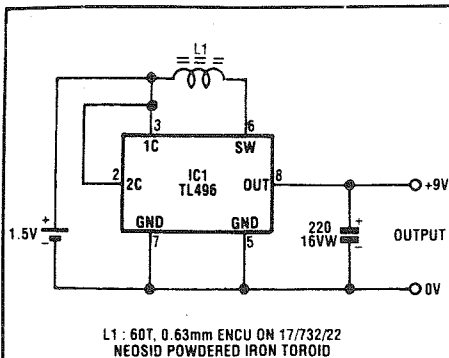

1.5V TO 9V DC CONVERTER

Fig.2: in addition to the IC, the final circuit uses an inductor, a single capacitor & a 1.5V battery. The circuit can also be powered from a 3V supply, in which case the connection to pin 3 is deleted.

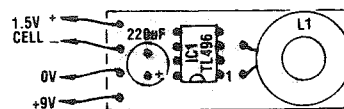


Fig.3: install the parts on the PC board as shown here. The inductor (L1) consists of 60 turns (approx.) of 0.63mm ECW on a small toroid core.

of 0.63mm diameter enamelled copper wire (ECW). To wind the inductor, first take a 2-metre length of wire and thread it half-way through the toroid core. The first layer is now wound using one end of the wire, followed by the second layer using the other end.

Keep the turns tight and as closely spaced together as possible. There should be about 60 turns total, although the exact figure is not critical.

Clean and tin the ends of the leads carefully before soldering the inductor to the board. The external leads to the 1.5V battery can be wired to a suitable 1.5V battery holder (optional).

When the assembly is complete, install the battery and measure the output voltage from the board. It should be very close to 9V.

Exercise extreme caution if you intend soldering a battery snap connector to the output terminals, to mate with an existing snap connector. In this case, you will have to connect the

terminals that have been salvaged from a discarded 9V battery. Check the output polarity carefully with your multimeter before connecting the project to any equipment.

Depending on your situation, you can use either an AA, C or D-size battery with the circuit. Table 1 shows the expected input currents for loads ranging from 0.1mA to 40mA. A D-size cell will last longer than AA or C cells, especially for high input currents, while alkaline cells will last longer than carbon zinc types.

Finally, you can modify the unit so that it functions as a 3V to 9V converter by cutting the track between pin 2 and pin 3 of the TL496 and also cutting the track between pin 3 and the coil (positive input side). Then place a small link from pin 2 to the coil (positive input side). This will not make the circuit any more efficient but because the input current is halved, will approximately double battery life.

TABLE 1

Load Current	Input Current
no load	50uA
0.1mA	1mA
0.5mA	6mA
1mA	12mA
2mA	25mA
5mA	65mA
10mA	134mA
20mA	250mA
40mA	460mA

red lead to the negative (-) terminal of the board and the black lead to the positive (+) terminal to ensure correct polarity at the battery snap terminals.

Alternatively, you can use output

Notes & Erratas

STORE LOCATIONS:

NSW • Albury 21 8399 • Bankstown Square 707 4888 • Blacktown 671 7722 • Brookvale 905 0441 • Bondi 387 1444 • Campbelltown 27 2199 • Chatswood Chase 411 1955 • Chullora 642 8922 • Gore Hill 439 5311 • Gosford 25 0235 • Hornsby 477 6633 • Hurstville 580 8622 • Kotara 56 2092 • Liverpool 600 9888 • Maitland 33 7866 • Miranda 525 2722 • Newcastle 61 1896 • North Ryde 878 3855 • Parramatta 689 2188 • Penrith 32 3400 • Railway Square 211 3777 • Sydney City 267 9111 • Tamworth 66 1711 • Wollongong 28 3800 **ACT** • Belconnen (06) 253 1785 • Fyshwick 80 4944 **VIC** • Ballarat 31 5433 • Bendigo 43 0388 • Box Hill 890 0699 • Coburg 383 4455 • Dandenong 794 9377 • East Brighton 592 2366 • Essendon 379 7444 • Footscray 689 2055 • Frankston 783 9144 • Geelong 232 7111 • Melbourne City 399 Elizabeth St 326 6088 & 246 Bourke St 639 0396 • Richmond 428 1614 • Ringwood 879 5338 • Springvale 547 0522 **QLD** • Brisbane City 229 9377 • Buranda 391 6233 • Cairns 311 515 • Chermiside 359 6255 • Redbank 288 5599 • Rockhampton 27 9644 • Southport 32 9033 • Toowoomba 38 4300 • Townsville 72 5722 • Underwood 341 0844 • **SA** • Adelaide City 223 4122 • Beverley 347 1900 • Elizabeth 255 6099 • Enfield 260 6088 • St. Marys 277 8977 **WA** • Cannington 451 8666 • Fremantle 335 9733 • Perth City 481 3261 • Midland 250 1460 • Northbridge 328 6944 **TAS** • Hobart 31 0800 **NT** • Stuart Park 81 1977

PHONE ORDERS SYDNEY AREA 888 2105 OUTSIDE SYDNEY (FREE CALL) 008 22 6610

STORES ACROSS AUSTRALIA & NEW ZEALAND

